

# Year 6: Electricity




## CREATING CIRCUITS AND UNDERSTANDING HOW DIFFERENT COMPONENTS AFFECT THEIR CAPABILITIES:

### How to draw simple circuit diagrams

Electrical circuits can be represented by simple diagrams.

There are recognised symbols for all the components in a circuit such as battery, bulb, motor, buzzer, and wire.

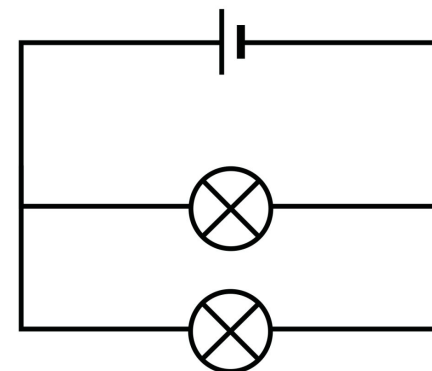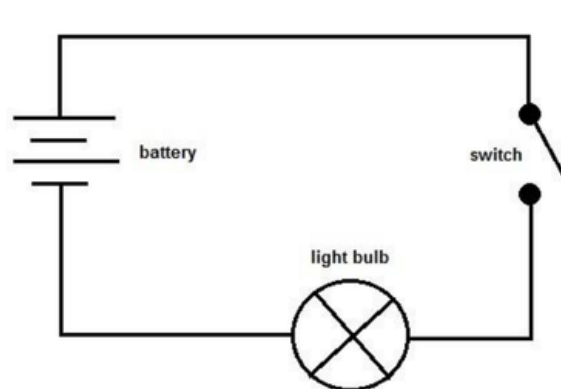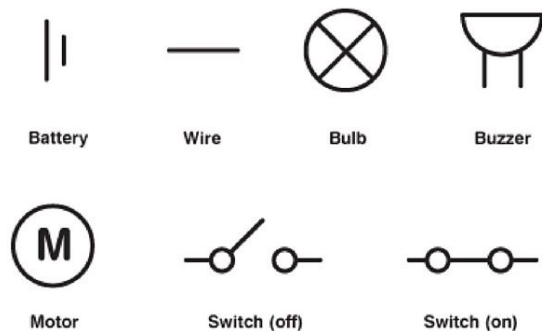Components need to be arranged in a specific way for a circuit to work.




### What does the voltage of an electrical current mean?

The voltage is what we use to measure the power of a cell to produce electricity; it is a measure of the push of electronic current.

As the number and voltage of cells in a circuit increases, the brightness of a bulb or the volume of a buzzer will increase.

If the voltage in a circuit is too high, it may overload the bulb or buzzer, which will lead to it breaking.

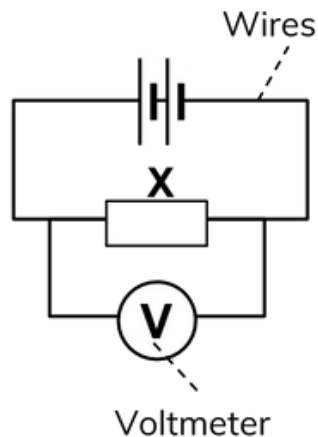High voltages are dangerous if precautions are not taken




### What affects how effective and electrical circuit is?

Two bulbs in a circuit can be wired up to create a series circuit or a parallel circuit.

If one bulb is removed in a series circuit the other will not shine as the circuit has been broken.

If one bulb is removed in a parallel circuit, there will still be a complete circuit for the other bulb so it will continue to shine.

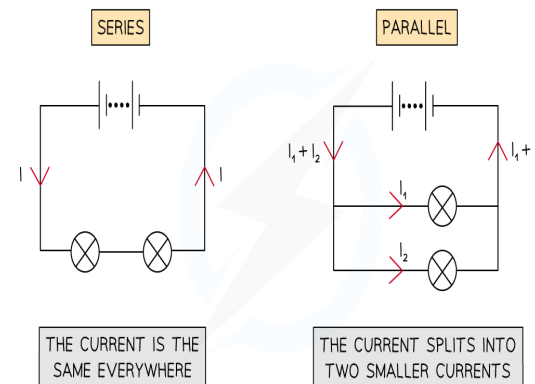We can use this knowledge to explain the advantages of using parallel circuits.



Copyright © Save My Exams. All Rights Reserved

## KEY VOCABULARY



**CIRCUIT:** a complete route which an electrical current can flow around



**CURRENT ELECTRICITY:** a flow of electricity through a wire or circuit



**PARALLEL CIRCUIT:** a circuit comprising of branches so that the current divides and only part of it flows through any branch



**SERIES CIRCUIT:** a circuit where all components are connected end-to-end to form a single path for current flow



**VOLTAGE:** the pressure from an electrical circuit's power source that pushes charged electrons (current) through a conducting loop